

**Electronics 315**  
**Practical 3 Report**

---

**Name:** Dean Jeggels

**Student Number:**23676787

**Plagiarism Declaration:**

By submitting this assignment with your name and student number filled in you agree with the following statements:

*“I have read and understand the Stellenbosch University Policy on Plagiarism and the definitions of plagiarism and self-plagiarism contained in the Policy [Plagiarism: The use of the ideas or material of others without acknowledgement, or the re-use of one’s own previously evaluated or published material without acknowledgement or indication thereof (self-plagiarism or textrecycling)].”*

*“I know that plagiarism is a punishable offence and may be referred to the University's Central Disciplinary Committee (CDC) who has the authority to expel me for such an offence.”*

*“I declare that, except where a source has been cited, the work contained in this assignment is my own work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.”*

---

**THIS REPORT COUNTS FOR A TOTAL OF 10 MARKS AND MAKES UP ONE THIRD OF THE OVERALL GRADE FOR THE PRACTICAL. TO GET THE MARKS FOR A SECTION, THE CONTENT MUST BE COMPLETE, COMPREHENSIVE AND MATCH THE RESULTS OBTAINED FROM THE SIMULATION TEST BENCH AND THE PRACTICAL DEMONSTRATION. IF ANY SECTION IS OMITTED, THE REPORT CANNOT SCORE HIGHER THAN 4/10.**

[illegible]

Resistor	Designed	Actual
R1	4k	3947
R2	1.2k	900
R2var	0-1000	300

R3	1.2k	1202
R4	25k	24.93k
R5	1M	1M
R6	640k	640k
R7	370k	390k
R8	12k	11.88k
RE8	1,1k	1077.8k
RC8	42k	41.767k
Ren	0.5	0.5
Rep	0.5	0.5
RE	120	118
<b>Capacitors</b>		
Cout	4700u	4700u
Cc1	10u	10u
Cc2	10u	10u
Cvcc	100u	100u
Cvee	100u	100u

**Table 1: Resistors, capacitors and transistor choices**


### **Power Amplifier Design:**

We first calculate the maximum voltage we can get using the 20V power supply.

We choose VRE and VREN to be 0.2V.

$$V_{o\_max} := V_{cc} - V_{ce5\_sat} - V_{be1\_on} - V_{be2\_on} - V_{RE} - V_{REN} = 17,9$$

For error margin we design for 17V ■

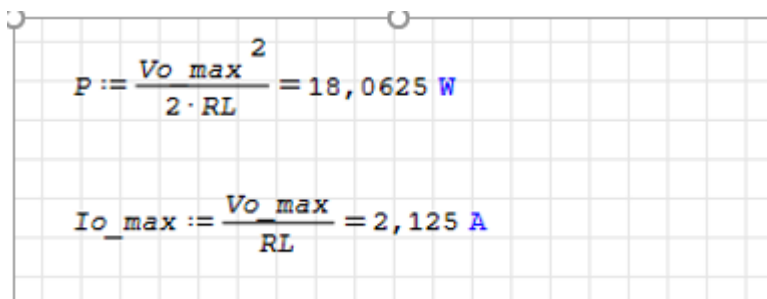

$$P := \frac{V_{o\_max}^2}{2 \cdot R_L} = 18,0625 \text{ W}$$

$$I_{o\_max} := \frac{V_{o\_max}}{R_L} = 2,125 \text{ A}$$

Here we see the maximum power we can achieve is 18W which meets specification requirements and the maximum current is 2.125A which also meets specification requirements.

Due to Darlington pair configuration we can calculate IB1(max) using Io(max).

We also choose ic6(min) to be small enough for it to be on.

$$i_{c6}(\min) = 0.6 \text{ mA}$$

$$i_{B1\_max} := \frac{I_{o\_max}}{(B1 + 1) \cdot B2} = 0,0004 \text{ A}$$

$$i_{C6\_max} := i_{C6\_min} + i_{B1\_max} = 0,001 \text{ A}$$

$$i_{B6\_max} := \frac{i_{C6\_max}}{B6} = 1,0208 \cdot 10^{-5} \text{ A}$$

$$I_{C5} := I_{R1} + i_{C6\_min} + i_{B1\_max} = 0,0015 \text{ A}$$

$$R_E := \frac{V_{RE}}{I_{C5}} = 131,5104 \Omega$$

Choose  $I_{R1} \gg i_{B6(max)}$

We thus chose  
 $I_{R1} = 500 \mu\text{A}$

Choose to design for  $R_E = 120 \Omega$  because of standard resistor values in lab.

$$R_B := 0,1 \cdot B5 \cdot R_E = 1200 \Omega$$

$$I_{B5} := \frac{I_{C5}}{B5} = 1,5208 \cdot 10^{-5} \text{ A}$$

$$V_{th} := V_{CC} - V_{RE} - V_{eb5\_on} - I_{B5} \cdot R_B = 19,0818 \text{ V}$$

$$R3 := V_{CC} \cdot \frac{R_B}{V_{th}} = 1257,7462 \Omega$$

Choose  $R3 = 1.2 \text{ k}\Omega$

$$R4 := \frac{R3 \cdot V_{th}}{V_{CC} - V_{th}} = 24936,6871 \Omega$$

Choose  $R4 = 25 \text{ k}\Omega$

### VBE-Multiplier:

$$V_{bb} := V_{be1\_on} + V_{be2\_on} + V_{be3\_on} + V_{be4\_on} = 2,6 \text{ V}$$

$$I_{R1} = \frac{V_{bb}}{R1 + R2}$$

$$R2 := 5200 \Omega - R1$$

$$V_{bb} = \left(1 + \frac{R1}{R2}\right) \cdot V_{be4\_on}$$

$$R1 := 4 \text{ k}\Omega$$

$$R2 = 1200 \Omega$$


We test the  $R2$  value in spice and lower it until it reached a high enough temperature operating temperature of at least  $130^\circ\text{C}$ . This got us to a new  $R2$  value of  $900 \Omega$ .

Safe Op. Area (@1kHz):	PASS	NULL	BJTs within SOA	BJTs inside SOA
T(power npn).....	PASS	NULL	Below 150 C....	132.318 C
T(power pnp).....	PASS	NULL	Below 150 C....	134.076 C

Then We choose  $R2$  in series with a variable resistor  $R2var$  of  $0-1000 \Omega$  which can later be adjusted in case of crossover distortion.

$$\begin{aligned}
 IB7_{max} &:= \frac{I_{c5}}{B7 + 1} = 1,5057 \cdot 10^{-5} \text{ A} \\
 IR6 &:= 2 \cdot IB7_{max} = 3,0115 \cdot 10^{-5} \text{ A} \\
 VB7_{max} &:= -(V_{eb4\_on} + V_{eb3\_on} + V_{eb7\_on}) = -2 \text{ V} \\
 R6 &:= \frac{V_{cc} + VB7_{max}}{IR6} = 5,9771 \cdot 10^5 \Omega \\
 R5 &= 1 \cdot 10^6 \text{ A}
 \end{aligned}$$

 We want the voltage at the base of Q7 to be -2V allowing the output to optimally and symmetrically swing. Using a R6 value of 600kΩ and spice analysis we found the value at the base of Q7 to be around -2.4V after adjusting R6 to 640kΩ we get a value closer to -2V and thus chose to design based off of that.



The resistance seen by the amplifier Rx was calculated as 9MΩ using small signal analysis this lead to a design choice of R5 = 1MΩ because it was the highest resistor obtainable from the lab choices.

### **Preamplifier Design:**

The preamp sees a load resistance of 360kΩ . We choose a 2N2219 transistor because of its high voltage gain. The input signals max current is limited to 1mA therefore we need a large input resistance and a common emitter configuration would be the best design choice seeing as it fits the specifications of large input resistance.

We need to choose a collector current for our transistor to design for. The current IC8 needs to supply enough current to load the input resistance of the power amplifier. Seeing as the resistance seen by the pre amp is very high the required current is very small and 0.5mA should be enough. Thus IC8=0.5mA

$$A_v := -\frac{V_o}{V_{in}} = -34$$

$$I_{B8} := \frac{I_{C8}}{B8 + 1} = 4,9505 \cdot 10^{-6} \text{ A}$$

$$R_{E8} := \frac{V_{cc} - V_{ee} - V_{ce5\_sat}}{I_{C8} \cdot (1 - 2 \cdot A_v)} = 1147,8261 \text{ } \Omega$$

$$V_{bb8} := V_{ee} + I_{C8} \cdot R_{E8} + V_{be8\_on} = -18,7261 \text{ V}$$

$$R_{C8} := R_{E8} \cdot (-A_v) = 39026,087 \text{ } \Omega$$

$$R_{th} = 0,1 \cdot (B8 + 1) \cdot R_{E8} = 11593,0435 \text{ } \Omega$$

$$R_{th} = \frac{R7 \cdot R8}{R7 + R8}$$

$$V_{th} = \frac{R8}{R7 + R8} \cdot (V_{cc} - V_{ee}) - V_{ee}$$

$$R7 := 370 \text{ k}\Omega$$

$$R8 := 12 \text{ k}\Omega$$

Adjusting RC8 to 42k $\Omega$  provides us with the best gain for our circuit and thus it was chosen to change the RC8 value to 42k $\Omega$ .

### **Frequency Analysis and Capacitor Design:**

The following results for the total harmonic distortion at full power for different frequencies were obtained from the spice analysis. This is within specifications and is thus satisfactory.

THD @ 1kHz (full pwr):	PASS	..1.	Below 4 %.....	1.67889 %
THD @ 40Hz (full pwr):	PASS	..1.	Below 4 %.....	1.46564 %
THD @ 20kHz (full pwr):	PASS	..1.	Below 4 %.....	2.63698 %

### **Capacitor design:**

#### **Low frequency cutoff:**


**Cc1:**

Our circuit should cut off frequencies lower or equal to 20Hz as set by the specifications.

We have been provided with 10 uF, 100 uF and 4700 uF capacitors.

We thus perform frequency analysis to see which of these capacitor would work best.

We first look at Cc1.

 

The capacitor sees the following equivalent circuit. The resistance  $R_{eq}$  can then be calculated as  $[R7 || R8 || (r_{\pi 8} + [\beta 8 + 1]R_{E2})]$ .

$$R_{eq} = 10.57 \text{ k}\Omega$$

For  $f_L = 20 \text{ Hz}$  we need a time constant  $\tau_{CC1} = 7.95 \text{ ms}$


$$\text{Thus using } \tau_{CC1} = C_{C1}[R7 || R8 || (r_{\pi 8} + [\beta 8 + 1]R_{E2})]$$

We get  $C_{C1} = 0.72 \text{ }\mu\text{F}$

This is far lower than our lowest provided capacitor of  $10\text{ }\mu\text{F}$ . However if we use  $C_{C1} = 10\text{ }\mu\text{F}$  we get a time constant of  $105.7 \text{ ms}$  which gives us a cutoff frequency of  $1.5 \text{ Hz}$ , which is still far within specifications and can thus be used.

**$C_{C2}$ :**

Equivalent circuit

 


$$\tau_{CC2} = C_{C2}(R_{IN} + R_C)$$

using the given capacitance of  $10\text{ }\mu\text{F}$  we get a time constant of  $\tau_{CC2} = 4.01 \text{ s}$

this gives us a cutoff of  $0.03959 \text{ Hz}$  which is well within specification

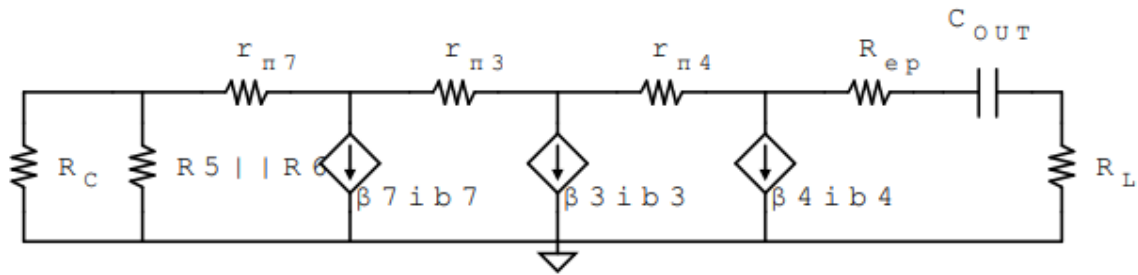**Cout:**

We will choose the Cout capacitor as 4700uF capacitor provided.



$$\tau_{OUT} = C_{out}(R_L + R_{ep} + \frac{\frac{r_{\pi 7} + (R_c || R_5 || R_6)}{(\beta_7 + 1)} + r_{\pi 3}}{(\beta_3 + 1)} + r_{\pi 4})$$

Calculating the time constant using the Cout value of 4700uF gives us  $\tau_{OUT} = 0.038s$ .

Which gives us a cutoff of 4.2Hz which is below the specification of 20Hz. Thus the capacitor of 4700uF would be sufficient for use.

**Gain Analysis:**


Theoretically we designed for an output voltage of 17V peak with a 0.5V peak input signal

$$A_v := - \frac{V_o}{V_{in}} = -34$$

However after some of the above values were adjusted and spice analysis we noticed a peak output voltage of 12.2V on the designed values.


This lead to a new gain of 24.4 after spice analysis.



 

**Figure 3.1**

Upon testing of the circuit in practice we got an output voltage of 12.8V pk-pk using the 10X probe to measure the output from a 0.5Vpk-pk 1kHz signal and thus a gain of 25.6. which agrees much more with the spice results obtained than the theoretical calculations.

 

**Figure 3.2**

## **Power and Thermal Analysis:**

### **Power Analysis**

For Transistors we use the equation:

$$P_Q = V_{CE} \cdot I_C$$

For Resistors we use the equation:

$$P_R = V_R^2 / R$$

Transistor	Power dissipated (mW)
Q1	41.3
Q2	4701
Q3	45.5
Q4	4115
Q5	29.7
Q6	3.26
Q7	27.3
Q8	5.60

Resistor	Power dissipated (mW)
R1	0.828
R2	0.386
R2var	1.16
R3	0.675
R4	14.59
R5	0.650
R6	0.728
R7	0.00373
R8	0.114
RE8	0.318
RC8	165
Ren	0.0327
Rep	0.0348
RE	0.33

We see that the maximum power dissipation in all the 2N2219A and 2N2905A are low , however the TIP41/42C transistors have a relatively high power dissipation compared to the rest. We will perform thermal analysis to see whether this high power dissipation has a significant effect on the way we design our circuit. No thermal failure for the resistors are expected as they all dissipate very low maximum power.

### **Thermal Analysis**

#### **2N2219A and 2N2905A**

We find that the junction to ambient thermal resistances of the 2N2219A and 2N2905A are 190 K/W and 292 °C/W respectively from the datasheets. We assume an ambient temperature of 30 °C.

## 2N2219A

$R_{th\ j-a}$	thermal resistance from junction to ambient	in free air	190	K/W
---------------	---	-------------	-----	-----

## 2N2905A

$R_{th\ j-amb}$	Thermal Resistance Junction-Ambient	Max	292	437.5	°C/W
-----------------	-------------------------------------	-----	-----	-------	------

$$\begin{aligned} \text{Thus } T_{2N2219A} &= \theta_{amb} + \theta_{2N2219A\ (j-a)} P_{2N2219A\ (max)} \\ &= 37.828\ ^\circ\text{C} \end{aligned}$$

AND

$$\begin{aligned} T_{2N2905A} &= \theta_{amb} + \theta_{2N2905A\ (j-a)} P_{2N2905A\ (max)} \\ &= 43.29\ ^\circ\text{C} \end{aligned}$$


The max operating junction temperature for the 2N2219A and 2N2905A are however  $200^\circ\text{C}$ , which is well above the calculated temperatures of the transistors. This means that heat sinks are not required to use for the 2N2219A and 2N2905A transistors.

## TIP41C and TIP42C

Calculating from datasheet and using the power derating curve.

$T_J$	Max. operating junction temperature	150	°C
-------	-------------------------------------	-----	----

 ( $T_{case} = 25^\circ\text{C}$ ; unless otherwise specified)



$$\theta_{j-c} = (T_j - T_c) / P = (150 - 25) / 65 = 1.92\ ^\circ\text{C/W}$$

$$\theta_{j-a} = (T_j - T_a) / P = (150 - 30) / 2 = 60\ ^\circ\text{C/W}$$

$$\text{thus } \theta_{c-a} = 58.08\ ^\circ\text{C/W}$$

at maximum power the transistors reach a temperature of

$$T_{TIP41/42C} = \theta_{amb} + \theta_{TIP41/42C(j-a)} P_{TIP41/42C(max)}$$

$$= 312^{\circ}\text{C}$$

However the max operating temperature of the transistors are  $150^{\circ}\text{C}$ . This means that the temperatures far exceed the max operating temperature we need to lower the thermal resistance between device and ambient and thus heat sinks will need to be implemented.

Assuming thermal paste is applied appropriately we can say  $\theta_{c-s} = 1^{\circ}\text{C/W}$ . The heat sink plates are specified as Aluminium plates, 80x50x2 mm.

Using online calculator and above specifications we get

$$\theta_{s-a} = 11.5^{\circ}\text{C/W}$$

thus

$$T_j = \theta_{amb} + (\theta_{j-c} + \theta_{c-s} + \theta_{s-a}) P_{Q(max)}$$

We can now calculate the new operating temperatures of our TIP41/42C transistors.

$$Q2 = 97.87^{\circ}\text{C}$$

$$Q4 = 89.33^{\circ}\text{C}$$

This falls within the operating temperature of  $150^{\circ}\text{C}$  and thus it is safe to use Q4 and Q2 with heat sinks. After spice analysis the following temperatures were obtained by running it through the testbench

Safe Op. Area (@1kHz):	PASS	NULL	BJTs within SOA	BJTs inside SOA
T(power npn).....	PASS	NULL	Below 150 C....	95.3583 C
• T(power pnp).....	PASS	NULL	Below 150 C....	97.1441 C

As we can see the spice code passed the valid operating temperatures and thus our calculations are valid and satisfactory. We assumed that it is thus safe to build our circuit.

## **Results and Conclusions:**

### **Results:**

Upon rigorously calculating all the above values and running the tests through spice it is safe to assume that we can build our circuit using all the above values. The practical circuit performed fairly close to our spice results with similar gain as well as temperatures not getting too hot and transistors and resistors not blowing up from thermal failure. Any discrepancies in values could be explained by varying beta values in some transistors compared to theoretically predicted values. The use of long wires to connect certain parts of our circuits where the magnetic fields running through the wires can have an effect on the e-fields of other wires not running through the same node. As well as longer wires having a higher resistance which in effect can affect the currents of our circuit.

Our spice results from the given testbench were as follows

Power amplifier test results			
Smoke test (Hard P/F): P/F.	....	..Hard limit...	.....Test result.....
Safe Op. Area (@1kHz): PASS	NULL	BJTs within SOA	BJTs inside SOA
T(power npn).....: PASS	NULL	Below 150 C....	95.3583 C
T(power pnp).....: PASS	NULL	Below 150 C....	97.1441 C
Test param. (scoring): P/F.	Mark	...Benchmark...	.....Test result.....
ii(max).....: PASS	..1.	Below 1 mA.....	0.0404621 mA
Psig(speaker) @ 40Hz : PASS	..1.	Above 8 W.....	12.4421 W
Psig(speaker) @ 1kHz : PASS	..1.	Above 8 W.....	12.6111 W
Psig(speaker) @ 20kHz: PASS	..1.	Above 8 W.....	10.2097 W
Psig(spkr) (vi=1mV)....: PASS	..1.	Above 0.5E-5 W.	5.37529E-05 W
Pwr efficiency @ 1kHz: PASS	..1.	Above 45 %.....	53.9605 %
THD @ 1kHz (full pwr): PASS	..1.	Below 4 %.....	1.67889 %
THD @ 40Hz (full pwr): PASS	..1.	Below 4 %.....	1.46564 %
THD @ 20kHz (fll pwr): PASS	..1.	Below 4 %.....	2.63698 %
THD @ 1kHz (vi=1mV)....: PASS	..1.	Below 0.2 %.....	0.00564239 %
FINAL RESULT.....: PASS	.10 .	... Achievement score: 126.973	

### **Conclusion:**

To conclude our circuit satisfied all the specifications required but could still be improved by pushing the limits of our circuit, better build to further improve the efficiency and get a closer result to our theoretically calculated circuit.